

CS2610 Computer Organization Laboratory

Lab - 5

Objective:

In this lab you will design a simple 4-bit ALU and analyse the efficiency in terms of processing delay and power consumption.

Problem:

In the previous labs you had already designed and analysed different 4-bit adders, subtractors and multipliers in Verilog.

- a) By choosing the best candidates from the above, design a 4-bit ALU to perform fast addition, subtraction, bitwise AND and bitwise OR operations. There should be a control unit to select the required operation.
- b) Using the designed 4-bit ALU, implement an 8-bit ALU to perform the same operations.

Post-lab:

Submit a post-lab report with your verified outputs and performance analysis.

All your submissions should be clear and concise.

Copied and late submissions will not be evaluated.