

CS2610: Computer Organization and Architecture

Lab 1

Objective:

In this lab you will analyse the efficiency of different adder topologies in terms of processing delay and power consumption.

Problem:

You are given two 4-bit unsigned numbers A and B in two 4-bit registers. You are required to implement the addition of A and B in Verilog for the below mentioned scenarios:

1. You are provided with 4 full adders and two 4-bit registers R0 and R1.
2. You are provided with only 1 full adder and two 4-bit registers R0 and R1.

Compare the performance of the two scenarios in terms of processing delay and power consumption.

Mandatory Submission:

- 1) A lab report (softcopy) is due on Sunday (20-01-2019) by 11:59 PM.
- 2) The report must be submitted via moodle.
- 3) The report must clearly describe your approach in solving the given problem, experiment results and conclusions.
- 4) Please use snapshots from the tool to discuss your findings.
- 5) **Strictly no Plagiarism!**
- 6) Late submissions will not be entertained.